

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

KC0JFQ presents:

ICARC FOX Transmitter 102-73181-10
Latest (probably the last) Fox Transmitter Design

[H t t p : //www.icarc.org/icarc_foxhunt.htm](http://www.icarc.org/icarc_foxhunt.htm)

[H t t p : //n952.ooguy.com/HamRDF/index.html](http://n952.ooguy.com/HamRDF/index.html)

[H t t p : //n952.ooguy.com/eagle/index.html](http://n952.ooguy.com/eagle/index.html)

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

WORK BACKWARDS!


RF amp ← Frequency Synthesizer ← Control

<http://n952.ooguy.com/eagle>

Presentation by KC0JFQ

Power level Bandwidth Implementation

<http://n952.ooguy.com/eagle>

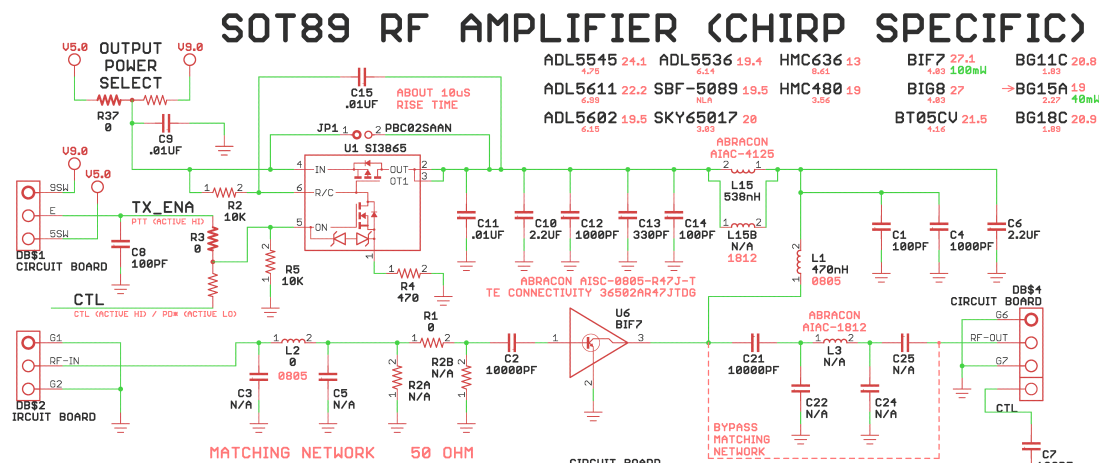


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Frequency Synthesizer Selection

Component life
Support Tools
Bandwidth

<http://n952.ooguy.com/eaglf>

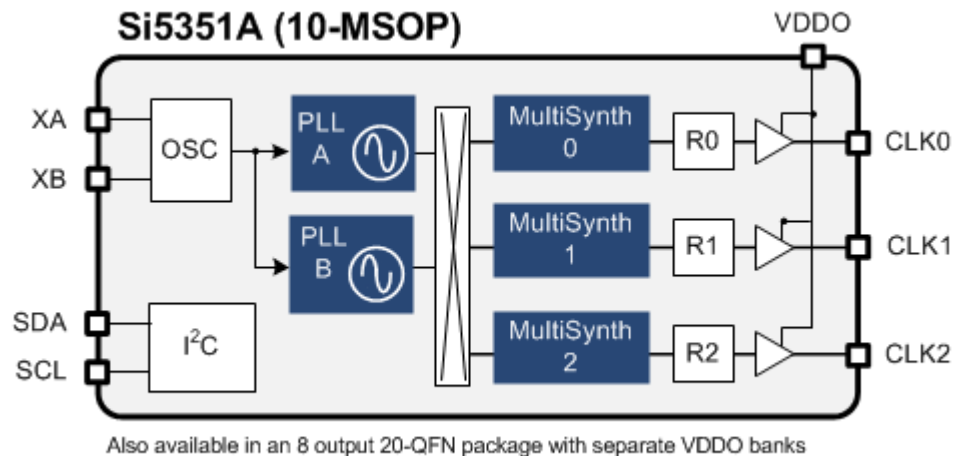

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ


Control System Selection

Raspberry Pi
ARM

SOC processor (ZiLOG ZNEO)

PIC processor (low cost)

<http://n952.ooguy.com/eagle>

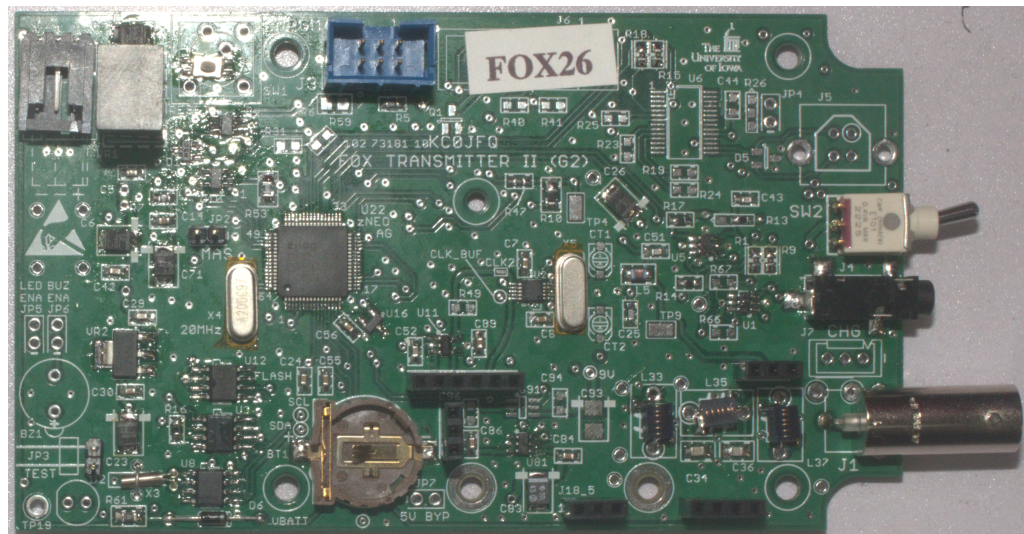


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware
FRAM/FLASH memory
TOY Clock

<http://n952.ooguy.com/eagle>

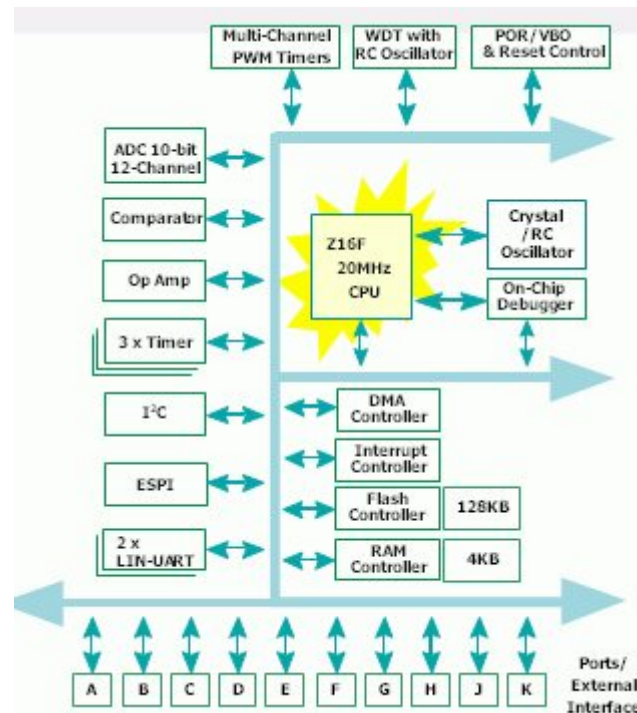

ICARC Fox Hunt Transmitter


Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware

Local Communications

<http://n952.ooguy.com/eagle>

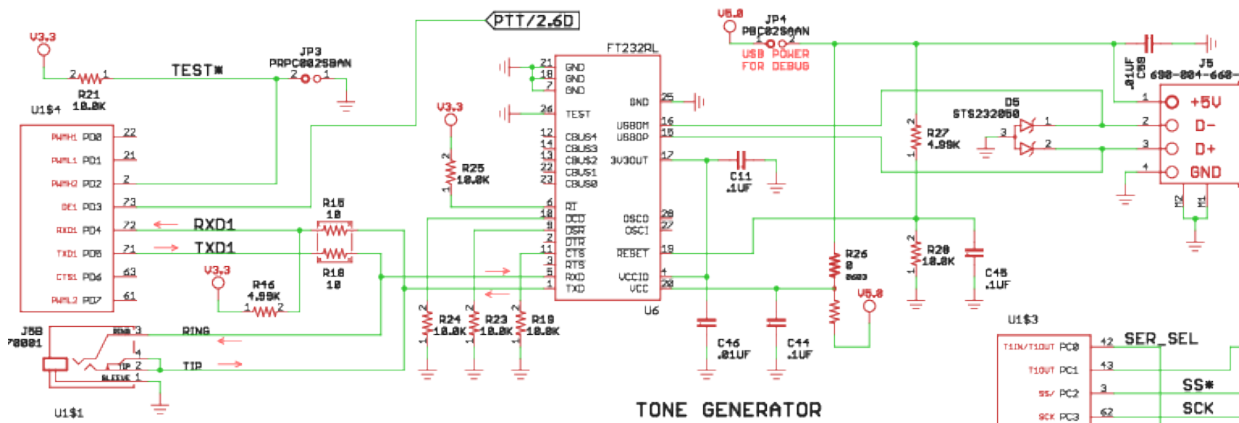


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware
TOY Clock



<http://n952.ooguy.com/eagle>

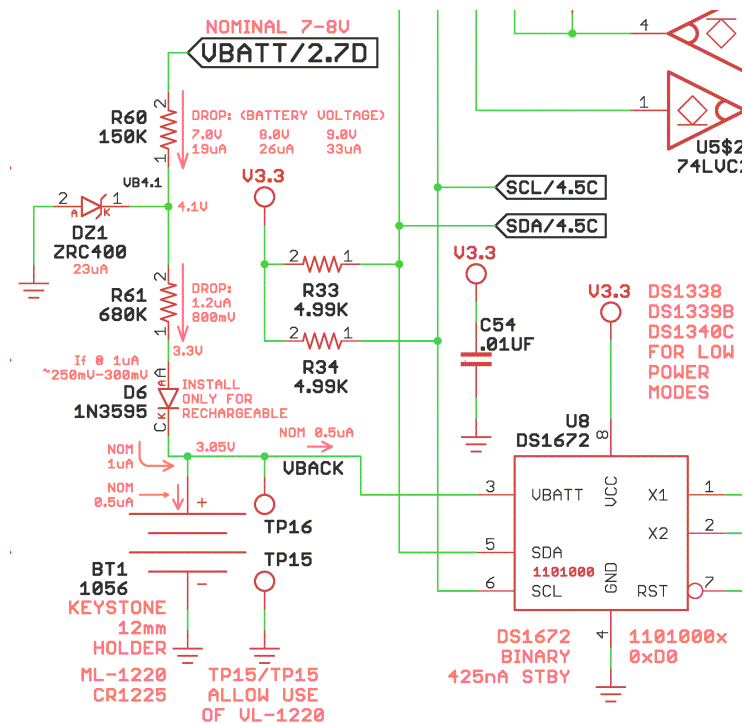

Presentation by KC0JFQ

Hardware

<http://n952.ooguy.com/eagle>

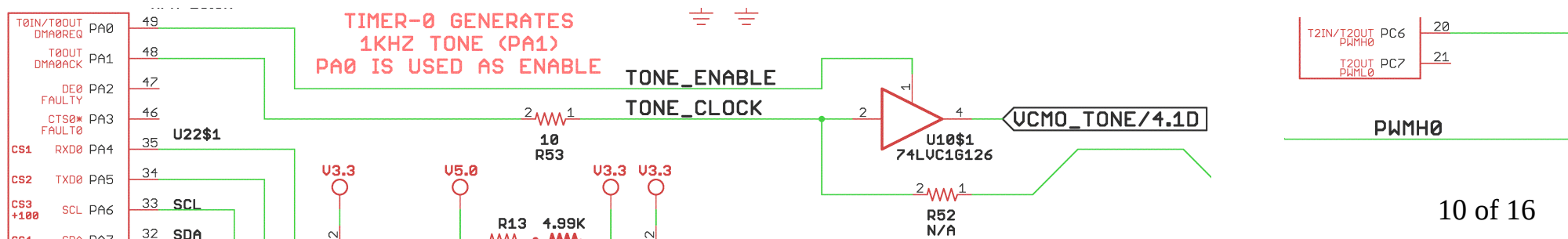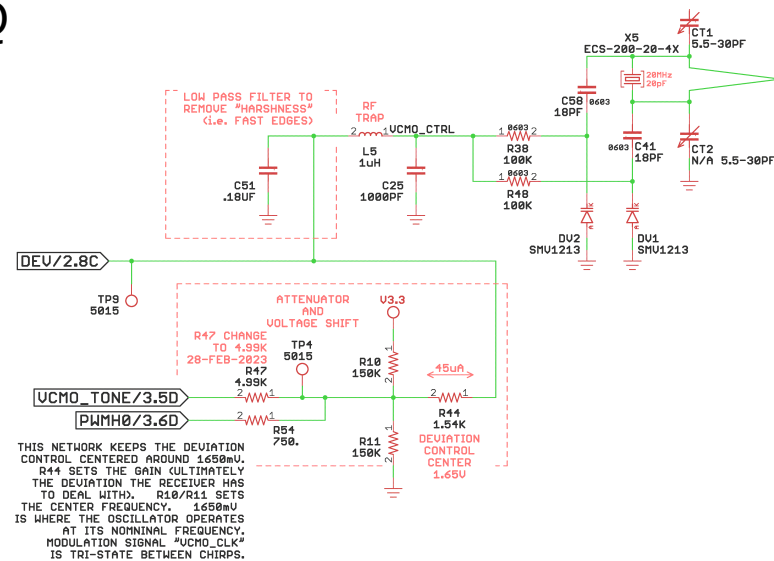


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware
Reference Clock

<http://n952.ooguy.com/eagle>

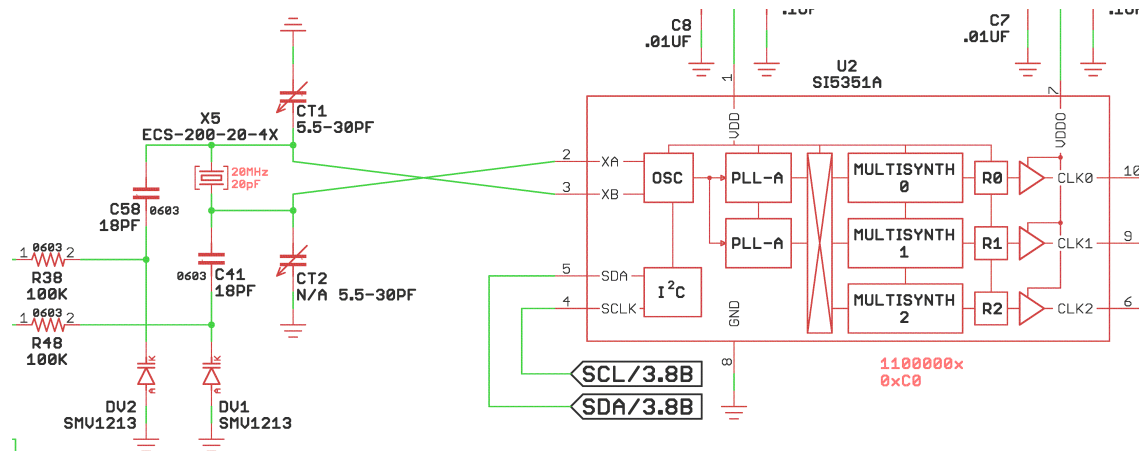

ICARC Fox Hunt Transmitter


Presentation by KC0JFQ

Control System

ZiLOG ZNEO

Hardware

Class C Amplifier

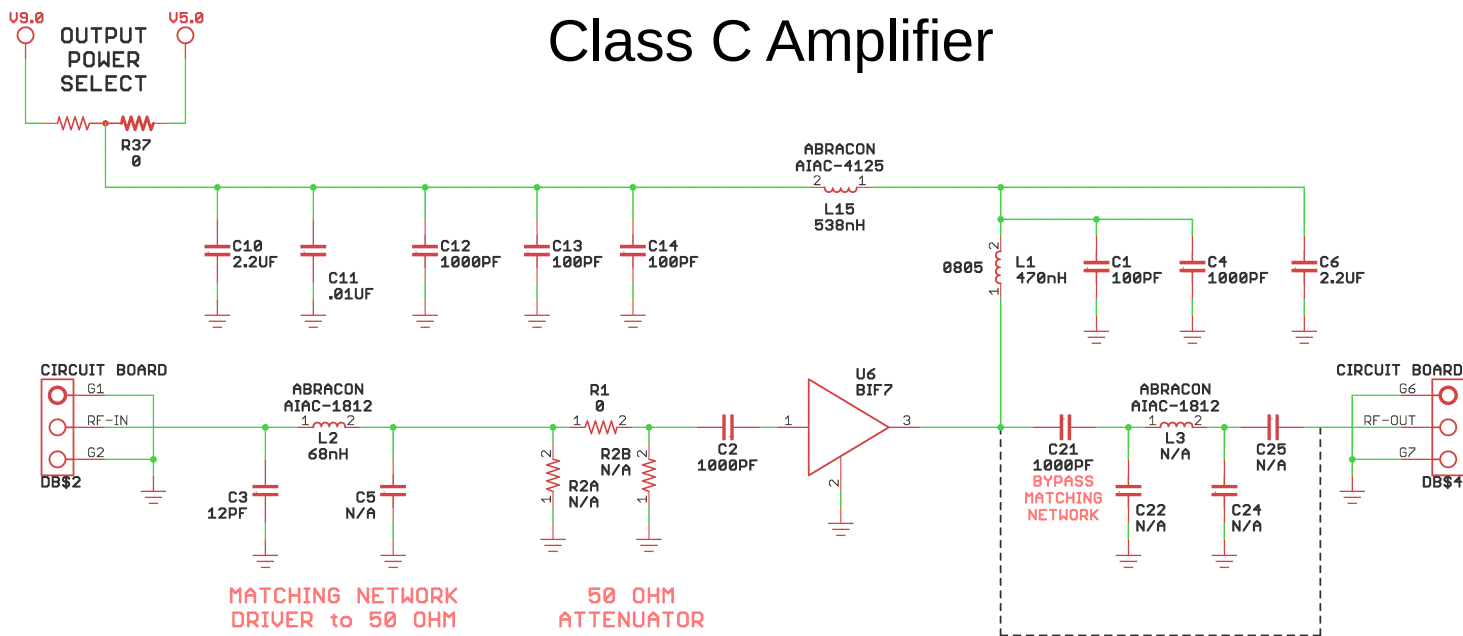

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ


Control System

ZiLOG ZNEO

Hardware

Switched Class-C Amplifier

SOT89 RF AMPLIFIER (CHIRP SPECIFIC)

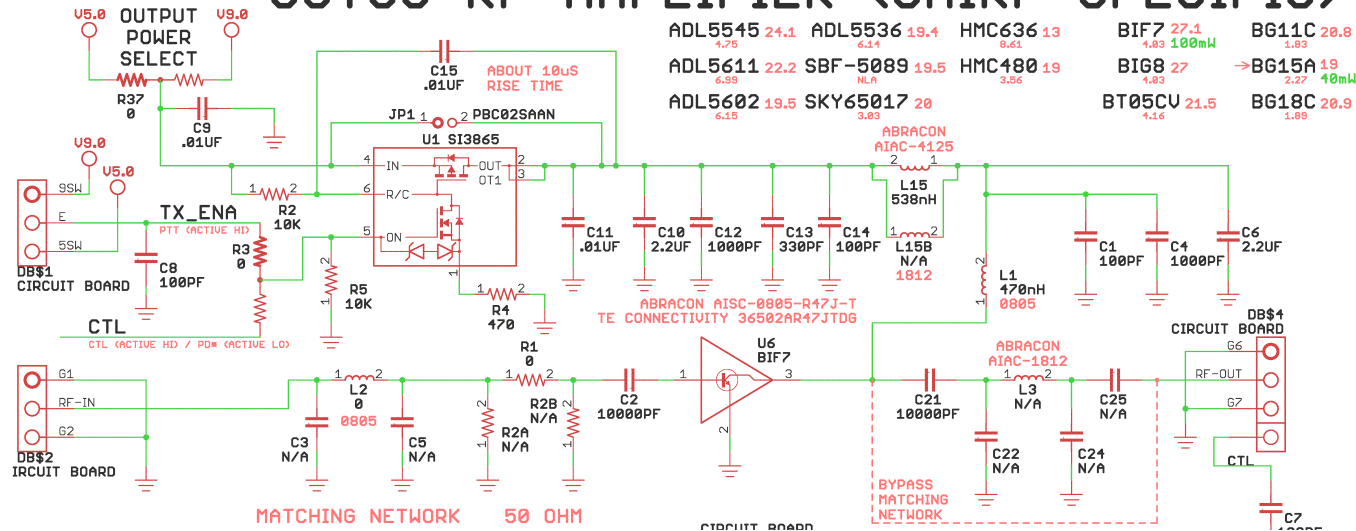


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System ZiLOG ZNEO

Hardware

Class D Amplifier

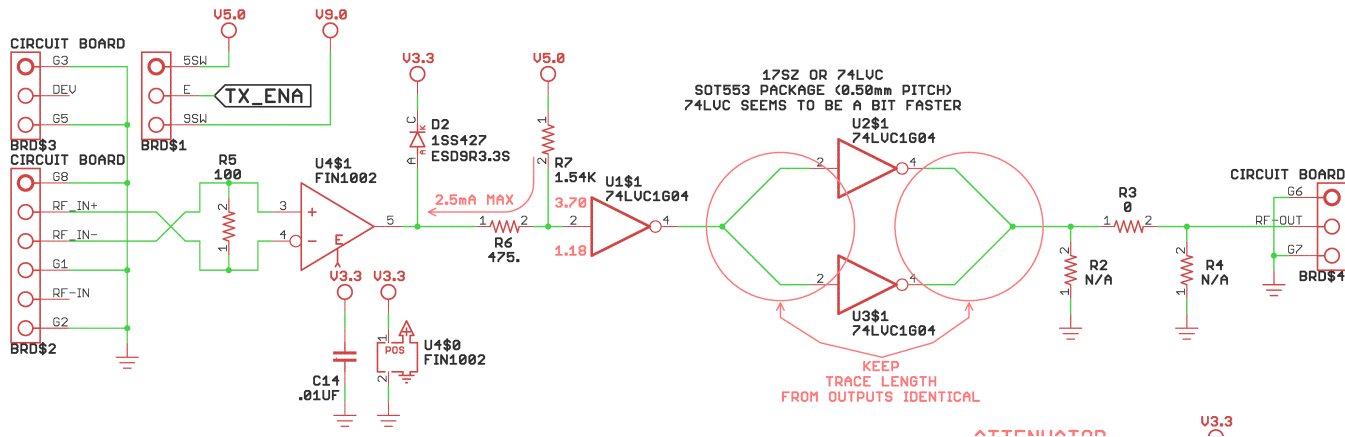


Presentation by KC0JFQ

Control System ZiLOG ZNEO

Hardware

RF transceiver module

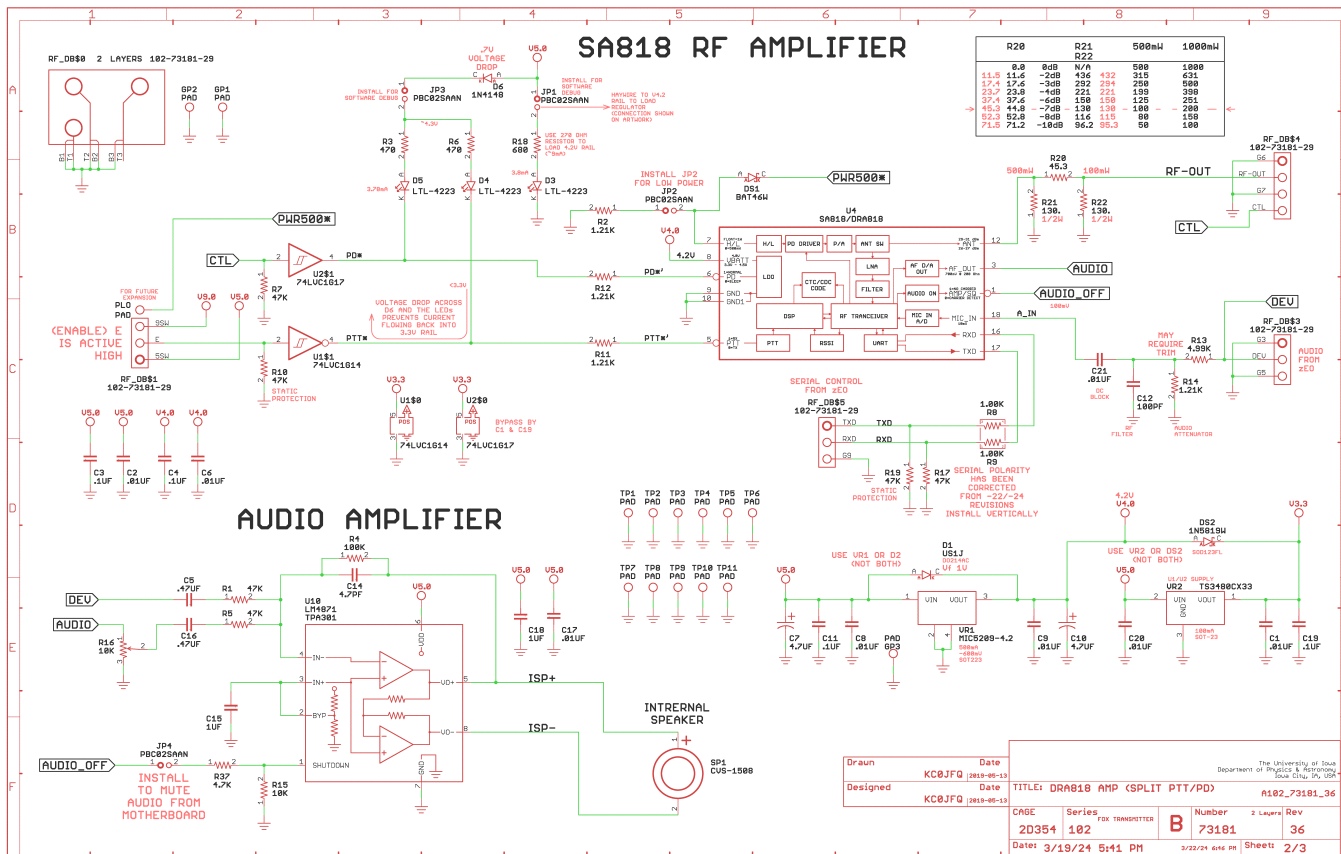


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware
No Amplifier at all

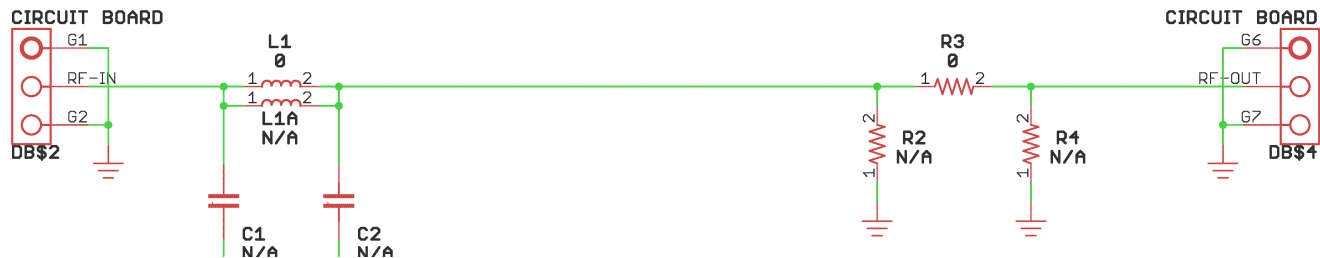

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

KC0JFQ presents:

ICARC FOX Transmitter 102-73181-10 Latest (probably the last) Fox Transmitter Design

[H t t p : //www.icarc.org/icarc_foxhunt.htm](http://www.icarc.org/icarc_foxhunt.htm)
[H t t p : //n952.ooguy.com/HamRDF/index.html](http://n952.ooguy.com/HamRDF/index.html)
[H t t p : //n952.ooguy.com/eagle/index.html](http://n952.ooguy.com/eagle/index.html)

1 of 16

Here we go again!

Discussion of ICARC FOX Transmitter by KC0JFQ

This is the culmination of a series of transmitters, with the goal of being easily configured for any style of fox hunting event.

ICARC currently has 12 of the latest revision transmitters.

Latest hardware and software development essentially complete. Incorporates all the features of the previous models. Adds more operating modes.

Successful hunt conducted with the new hardware 4/2024.

TWELVE 102-73181-10 units!

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

WORK BACKWARDS!

RF amp ← Frequency Synthesizer ← Control

<http://n952.ooguy.com/eagle>

2 of 16

We'll work backwards as I think that will make life easier.

These are battery powered (of course) so battery life can be an issue. Has to last through the entire event. Don't want to be buying batteries for each event. Will talk about battery selection towards the end.

Presentation by KC0JFQ

- Power level
- Bandwidth
- Implementation

[illegible]

All require low pass filter to suppress harmonics (LPF is on the motherboard).


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Frequency Synthesizer Selection

Component life
Support Tools
Bandwidth

<http://n952.ooguy.com/eagl>

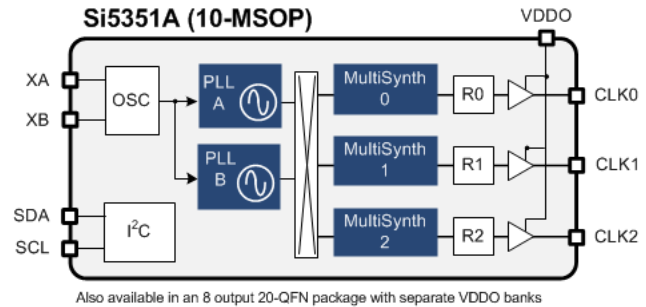

4 of 16

Pick one and it will likely be obsolete next year :-)

ICS525 and ICS307 were used in early units, none are available any longer ☹ (they kinda sucked anyway...).

Switch to SI5351 in the 102-73181-5 ☺. It is in production and far more flexible (i.e. programmable) than the ICS525/ICS307. Can hit all the 2M frequencies. Frequency calculation a bit involved, but the register values are pre-calculated with the resulting values saved in program flash in the Fox Transmitter System.

A frequency counter is useful when generating register patterns for the SI5351! (i.e. check your work and).

SA818/DRA818 is a low-cost (<\$15.00) RF transceiver module. Output 500mW or 1000mW. We program this with very simple ASCII text string. (most seem to be way less than 500mW).

A utility was produced to calculate the register values for the SI5351 multi-synth. Small table in zNEO flash, we can load anything through the serial port (or from FRAM).

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ


Control System Selection

Raspberry Pi
ARM

SOC processor (ZiLOG ZNEO)

PIC processor (low cost)

<http://n952.ooguy.com/eagle>

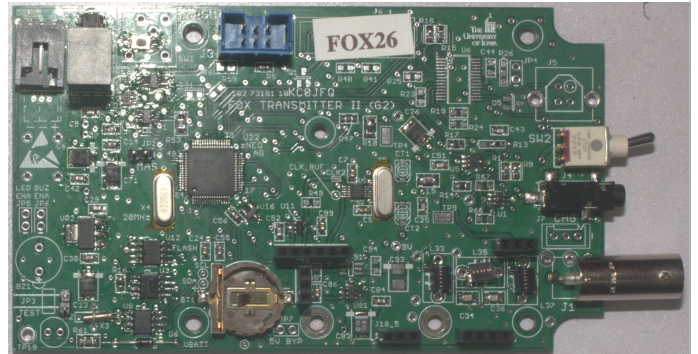

5 of 16

Large universe of SOC devices to choose from.

The ZiLOG ZNEO is what I settled on. This device implements a Harvard bus architecture with a VonNeumann address space. Split instruction and data (i.e. separate FLASH and RAM datapath) for access concurrency, with an instruction set that doesn't access these two spaces with different instructions (compiler-friendly).

The ZNEO selection is an outgrowth of the RIME/REASON GSE that started out life using a ZiLOG eZ8 processor (pure Harvard architecture). Software was getting too complex when dealing with Harvard-isms. This forced a change to ZNEO mid-stream (chip pinouts on the eZ8 matched the ZNEO saving circuit board rework).

All the 73161/73181 Fox Transmitter systems use the ZNEO.

The 102-73181-10 revision changes zNEO packages (now a 64 pin LCC) due to availability.


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware
FRAM/FLASH memory
TOY Clock

<http://n952.ooguy.com/eagle>

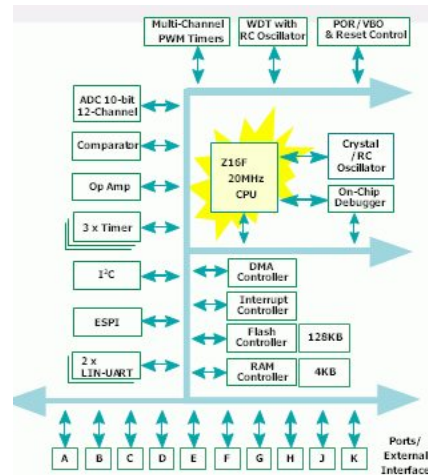

6 of 16

The ZNEO has 128KB of program flash and 4KB of data RAM (currently the control program is over 100K!).

ZiLOG provides development tools: c-compiler and linker and a low-cost programming device (ethernet connection to host). The build environment is hosted on a Linux box (using WINE).

External to the ZNEO are two *serial* memory devices, one FRAM and one FLASH. The operating schedule (commands) is in FRAM (easy/fast to change, but \$\$. \$\$) and the audio clips are in FLASH (large device for less than \$1.00).

These two device live on the zNEO SPI bus. The ZNEO provides the bus controller that is used to access these two devices.

Clock chip uses a 32,768Hz oscillator and a 15+32 bit counter. 15 bit counter divides the 32KHz to 1HZ and the 32 bit counter counts seconds from some epoch. Backup battery (coin cell) is charged by the main battery at a verrrrrrry low rate (less than 1uA). Main battery keeps backup cell from discharging. Clock allows set & forget Foxhunt setup!


ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System ZiLOG ZNEO

Hardware Power Conditioning Power Monitor

<http://n952.ooguy.com/eagle>

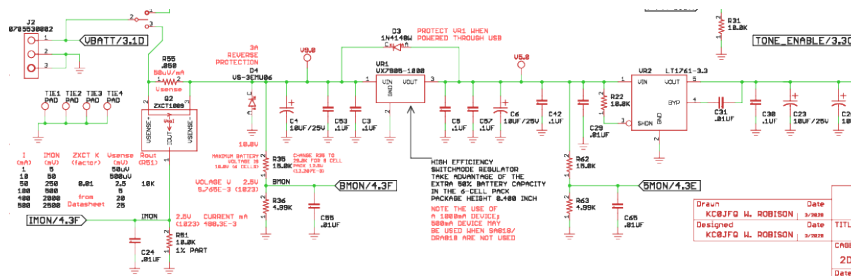

7 of 16

The system is powered by a six to twelve cell battery pack. Nominally a 6-cell AAA pack fits in the housing. A rechargeable pack could also be used.

A switch mode converter is used to produce the main 5V rail to minimize heat and wasted battery power (efficiency north of 90%). Device VR1 must be selected to supply adequate power to the RF daughterboard (DRA818 is a power pig).

A current sense circuit (Q2/R55) measures current from the battery, and voltage (R35/R36) at the battery. There is an additional voltage sense on the 5V rail (R62/R63).

3.3V for the ZNEO is provided by a low-cost low-dropout **linear** regulator (VR2). ZNEO is the primary load on the 3.3V rail. Logic gates on the motherboard are also powered by the 3.3V rail.

The RF daughterboard receives the regulated 5V rail and the raw battery voltage (both are switched). RF section is powered only during transmit.

The SA818/DRA818 take forever to wake up following application of power.

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ


Control System

ZiLOG ZNEO

Hardware

Local Communications

<http://n952.ooguy.com/eagle>

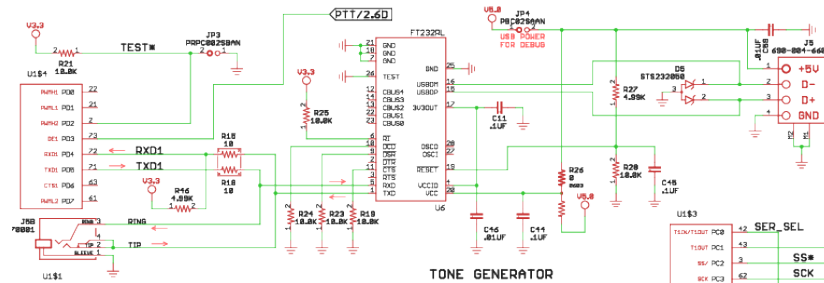

8 of 16

Connection to a host system (for FRAM/FLASH programming) is provided using one of the ZNEO serial ports (UART1).

This control port may be implemented as a USB serial port (J5) or a simple buffered Tx/Rx pair (J4). USB uses the FTDI FT232RL device. Use a USB to serial converter cable to connect to the buffered port (lower cost, easier to use).

A second serial port is buffered and routed to the daughterboard. This second serial port is dedicated to controlling the daughterboard (i.e. the SA818/DRA818 or an external **tranceiver**).

There was a network time function that appeared on previous models, it has been deprecated (never used it in the field). UART0 talks to SA818/DRA818. The 3.5mm port on motherboard (that was the network time function previously) now accesses UART1. Setup is much faster when you don't have to open the case!

FTDI cable: **TTL-232R-3V3-AJ**

Presentation by KC0JFQ

Hardware TOY Clock

NOMINAL 7-9V
UBATT/2.7D

R60 150k
 DROPS (BATTERY VOLTAGE)
 7.8V 8.8V 8.8V
 1.8uA 2.5uA 3.3uA

UB1.1
D21 ZRC400
 23uA

R61 680k
 DROPS 1.2uA 1.8uA
 3.3V

INSTALL ONLY FOR RECHARGEABLE
D6 1N3595

3.3V
 1uA
 ~250uA-300uA

NON 1uA 8.5uA
UBACK

TP16
TP15

BT1 1056
 KEYSTONE
 12mm
 HOLDER
 ML-1220
 CR1225

TP16/TP15
 ALLOW USE
 OF VL-1220

U3.3
R33 4.99k
R34 4.99k

SCL/4.5C
SDA/4.5C

U3.3
C54 .01uF

U8 DS1672
UBATT
UCC
X1
X2
SDA 1101000
SCL
RST

DS1672
 425nA STBY

1101000x 8xD0

DS1338
DS1339B
DS1340C
 FOR LOW
 POWER
 MODES

U5\$2 74LUC:

Operating schedules rely on the time from the TOY clock. So the TOY would normally be set the night before. Uncorrected drift is limited to a few seconds per day. All the TOY clocks are synchronized, so no additional synchronization is required at the fox hunt! Turn on the transmitter, listen for the **alive** message, and you're free to move on to the dropping the next station.

ICARC Fox Hunt Transmitter



Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware

Modulation/Deviation Control

<http://n952.ooguy.com/eagle>

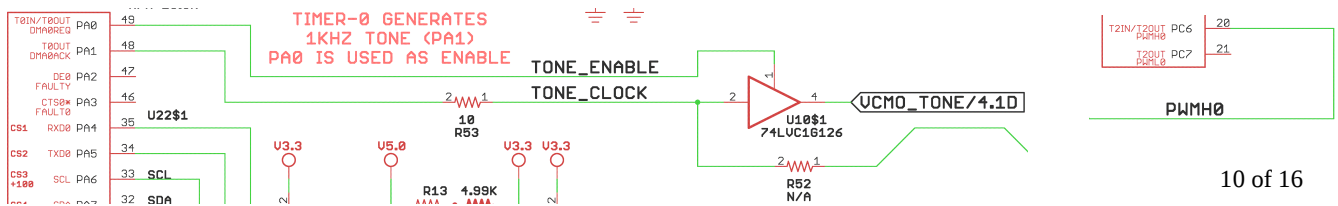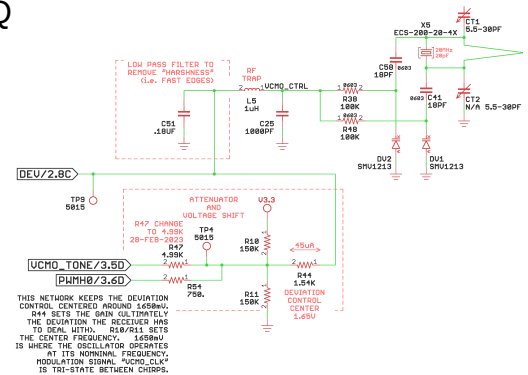

The ZNEO provides for two methods of supplying audio to the RF deviation control.

One is a simple square wave from a programmable clock/timer source in the ZNEO. This tone is gated through a buffer (U10) to allow for simple on-off control using a single port bit (this is the CW audio tone generator). The **TONE_ENABLE** signal is also used in other parts of the circuit, so it's not quite overkill.

A PWM controller (lower right corner) in the ZNEO may also be used to control the transmitter deviation.

The data stream to control the PWM channel is stored in the FLASH device. Byte samples are read from the FLASH and written to the upper 8 bits of the PWM register. Sample rate is controlled by setting the SPI clock rate. Latest software deals with rates of 4K, 5K, 8K, 10K, and 16K samples/second (we normally use a sample rate of 4KHz in the ICARC transmitters).

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ


Control System

ZiLOG ZNEO

Hardware

Reference Clock

<http://n952.ooguy.com/eagle>

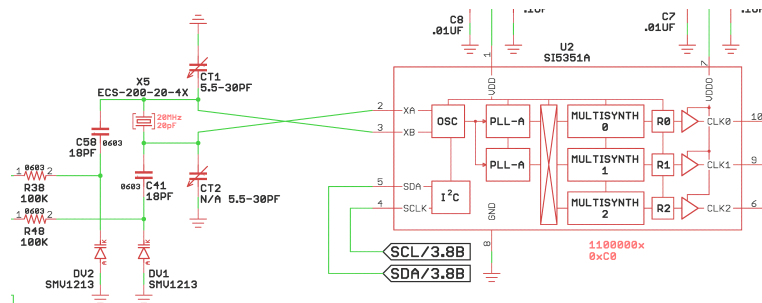

11 of 16

The reference clock for the SI5351 comes from a low-cost crystal (20MHz to match the ZNEO crystal). The load capacitors on the crystal are varactor diodes (i.e. voltage controlled capacitors or PIN diodes). The deviation control signal reverse biases the diodes which affects the junction capacitance thereby pushing and pulling the crystal frequency.

The SI5351 PLL chases the (varying) reference clock (X5) producing the FM modulation of the carrier. The output of the SI5351 is fed to the daughterboard for further amplification.

One channel is raw from the SI5351.

The second channel is buffered and level shifted to 5V.

These first two channels share a connection to the RF daughterboard.

The third is buffered through an LVDS driver.

ICARC Fox Hunt Transmitter


Presentation by KC0JFQ

Control System

ZiLOG ZNEO

Hardware

Class C Amplifier

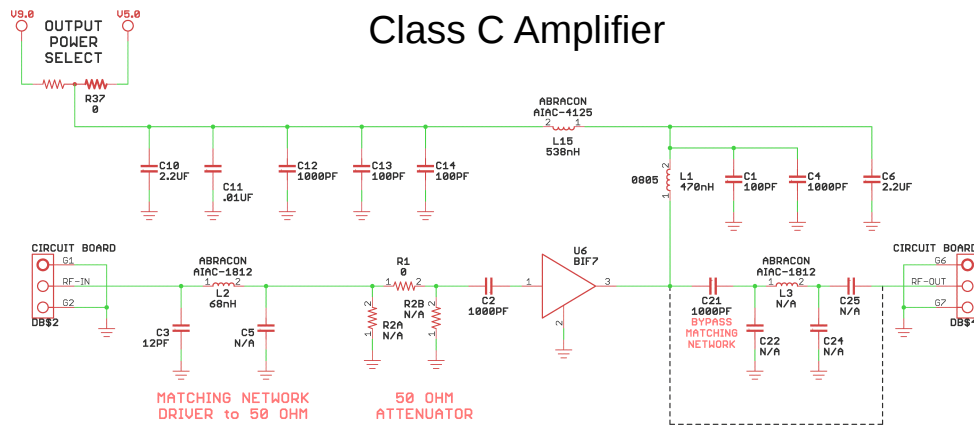

12 of 16

The RF daughterboard sits above the output filter on the motherboard.

One connector (DB\$1 is not shown) provides switched power, both the regulated 5V rail and the unregulated battery voltage.

The RF comes from the motherboard (DB\$2) and is routed to the gain block through an impedance matching network (C3, C5, L2), and attenuation network (R1, R2A, R2B), and a blocking capacitor (C2).

The output of the gain block is passed through another impedance matching network (C22, C24, L3) and the back to the low pass filter on the motherboard. The antenna connector (BNC) on the motherboard sits after the LPF.

This amplifier is capable of producing over 100mW when connected to the SI5351.

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ


Control System

ZiLOG ZNEO

Hardware

Switched Class-C Amplifier

SOT89 RF AMPLIFIER (CHIRP SPECIFIC)

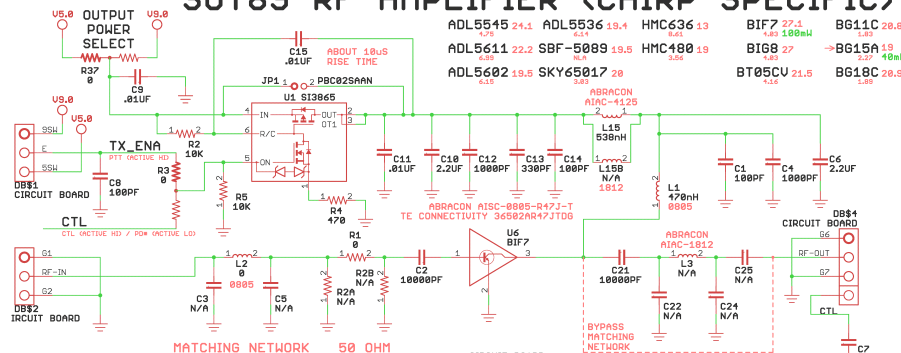

13 of 16

This RF amplifier, almost identical to 103-73161-28, is used to emulate a wildlife tracker and to operate A1A. The power to the RF gain block is switched by U1. The tracker mode is enabled using the **CHRP** command which causes the PTT*/TX_ENA signal to be asserted only when a chirp is being sent. Quiet time between chirps does not send RF.

The transmitter may operate in A1A mode using the **CONF CW** command and disabling audio modulation using the **FREQ 0.0** command.

The power switch (U1) is setup to *soft start* to limit the transient load presented to the 5V regulator on the motherboard and to soften the RF switching.

Like the other Class-C amplifiers, there are matching networks on input and output as well as an input attenuation network. The list of gain blocks (all are MMICs) are all 50 ohm input and output. The SI5351 output can be configured as a 50 ohm source.


This amplifier produces from 40mW(BG15A) to over 100mW(BIF7) when connected to the SI5351.

The 74LVC1G04 gate is carefully chosen for very low propagation delay (try a Diodes Incorporated 74LVC1G04W5-7) as we operate the gate at 150MHz, at the very edge of its performance envelope. Signals out of the 74LVC1G04 exhibit poor rise times, but this reduces higher order harmonics, which is to our advantage.

ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

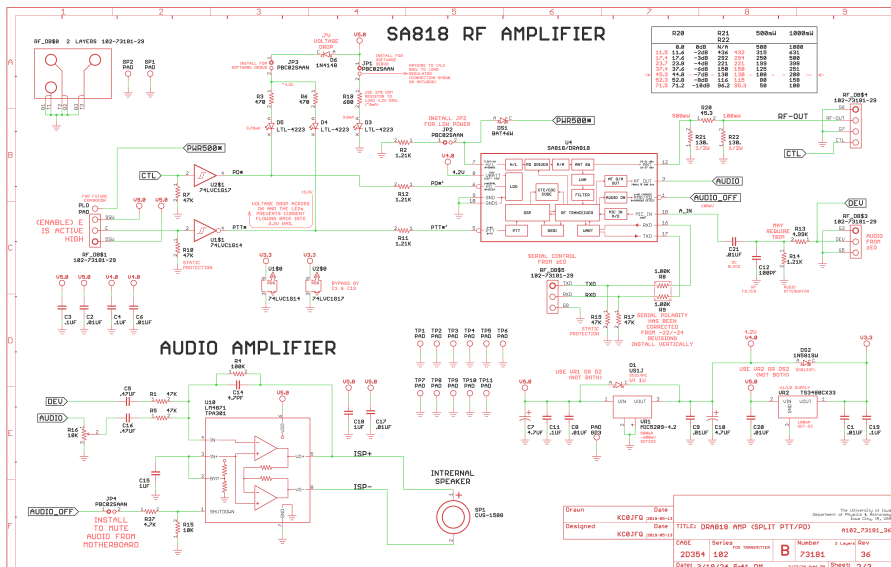Control System
ZiLOG ZNEO
Hardware
RF tranceiver module




ICARC Fox Hunt Transmitter

Presentation by KC0JFQ

Control System
ZiLOG ZNEO

Hardware
No Amplifier at all

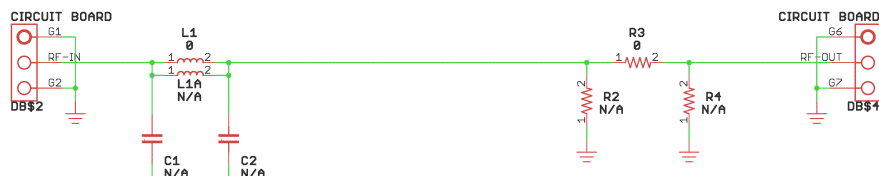

16 of 16

The synthesizer output may be run *naked*, right out to the antenna through the low pass filter on the motherboard using this board.

The board has an impedance matching section and an attenuator section, either of which may be bypassed.

The board also has a 5V monitor LED that can be useful in debugging hardware issues and for software development.

Due to the way RF is managed, the **wildlife tracker** and **A1A** operation is not possible with this daughterboard.