FOUR PORT UART

Presentation by KC0JFQ

KC0JFQ: William Robison

October 6, 2025

4-Port USB UART 102-73226-3 Current Design

http://n952.ooguy.com/HamRDF/index.html http://n952.ooguy.com/eagle/index.html

Job: fox present 15 File: fox present 15.tex



Table of Contents



Motivation

The MAIN Board

zNEO/eZ8 Programmer daughtercard

CI-V 3.5mm daughtercard

DE9M daughtercard

RS485 daughtercard

SPI daughtercard

Secret Content Section



Motivation




Why did I do it?

Interesting project
Individual serial connections growing out-of-contol
Condense to one box (and USB connection) on the bench
Easy/cheap to implement new physical interface

The MAIN Board



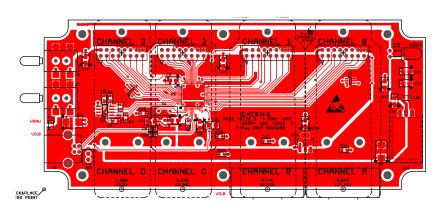Main-Board design for a multi-use USB UART




Hammond 1599E case



The Main Board



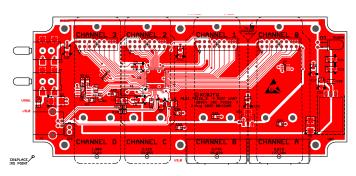

Plug-in Channel Card holds the actual interface

All cards are mechanically identical


Any cards may sit in any slot subject to width restrictions!

Channel 0 and 1 are a bit wider to accommodate DE9



The Main Board Schematic



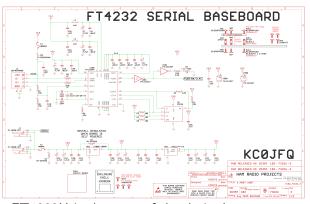

FTDIchip FT4232H is the guts of the design!

BUS Powered or Self Powered (on board power system)

TWO power jacks for **self powered** operation (daisy chain with other things)


 $93LC66B \ EEPROM \ holds \ programmable \ \textit{identity}$

Board spacing is nominally 12mm



The Main Board Channel Schematic



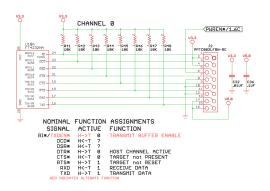

FOUR identical channels are in the FT4232H

Straight connection between FT4232H and daughtercard **PWREN*** goes low when USB host connects Full modem signals on all channels +5V and +3.3V to daughter card



zNEO/eZ8 Programmer





16-pin connector to main board.

Target Reset (button)

Logic-level buffers

6-pin programming header LED illuminates when host accesses this channel


Load Operating Software into the ICARC Fox Transmitters





zNEO/eZ8 Programmer Schematic



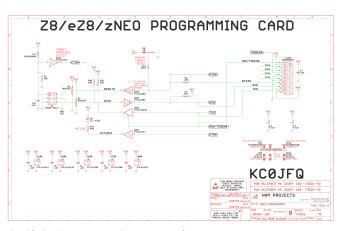

Simple half-duplex open-drain interface to target

TxD is tri-state to improve drive when host has programming bus

DTR active when host is connected (LED on) Reset button to alleviate frustration!



CI-V 3.5mm





16-pin connector to main board.

Logic-level buffers

Jumpers for FDX or HDX operation

3.5mm serial connection (ICOM CI-V compatible)

ACTIVE LED when host accesses channel


TX_DEN LED when output buffer active

Host access port on the ICARC Fox Transmitters (time, sequence, audio file)



CI-V 3.5mm Schematic



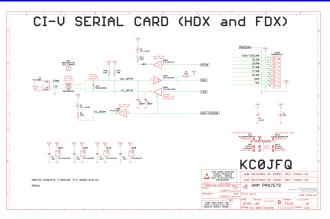

Same style half-duplex open-drain interface

TxD is tri-state to improve drive when host drives the bus

DTR active when host is connected (LED on)

JP1 allows quick Txd/RxD swap

JP2 allows CI-V operation







16-pin connector to main board.

Integrated RS232 buffers

DE9 male connector

DTR LED when host accesses channel


DTR also on the DE9 connector

PC-AT serial connector, standard pinout, standard voltage levels



DE9M Schematic



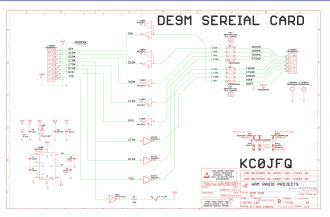

MAX3241 tranceiver provides charge pump for -V (all in one chip!) J1/J2/J3 jumpered straight across for PC-AT pinout (DCE) J1/J3 can be rewired to provide DCE pinout Output levels are +V and -V J2 is ground





16-pin connector to main board. Isolated supply

Optical Isolators and buffers

RJ45 network connector

ACTIVE LED when host accesses channel

NO power to network!


(PAD to power pin on bottom side)

KC0JFQ sensor network



RS485 Schematic



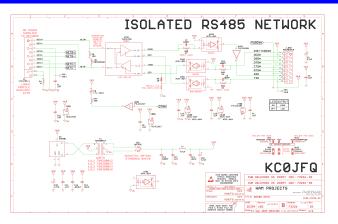

Optically Isolated RS485 network interface Low power isolation supply (driver, transformer, diodes) Opto-isolator device is logic-level output Keeps the DTR LED from other boards





16-pin connector to main board.

Buffers

MPSSE available **only** on Channel 0 and Channel 1 Bit-Bang available on all channels

DTR LED when host accesses channel


10-pin programming connector

Example for using MPSSE feature of FT4232H




SPI Schematic



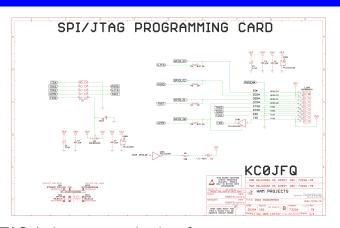

${\sf SPI/JTAG}\ device\ programming\ interface$

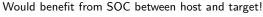Requires D2XX driver (PITA on Linux)
Pinput from 2010 vibntage ACTEL FPGA development kit





Secret Content



End of the line We are done here

Go away Get Back

Dragons be here

You are not permitted to lokk beyond here

Scary Notes for the Presenter

Notes taken from the Libreoffice presentation

Here we go again!
-Dolly Parton

Outline

Discussion of 4-Port USB UART by KC0JFQ

This is a simple USB UART design.

The slides should be pretty much self-explanatory